

{ {<P=41><C=06><S=extension><T=MC><M=2><L=1><X=F><id=001> } }

4161001

**F E** A sinusoidal a.c. flows through a resistor and the mean power dissipated by the resistor is  $P$ . If the frequency of the a.c. is doubled, which of the following expressions gives the new mean power dissipated by the resistor?

- A  $P$
- B  $\sqrt{2} P$
- C  $2P$
- D  $4P$

{ {<P=41><C=06><S=extension><T=MC><M=2><L=1><X=F><id=002> } }

4161002

**F E** A steady voltage  $V$  and a sinusoidal alternating voltage with peak value  $V_0$  is applied in turn to a resistor. The average power dissipated is the same in both cases. What is the relationship between  $V$  and  $V_0$ ?

- A  $V_0 = \frac{V}{2}$
- B  $V_0 = \frac{V}{\sqrt{2}}$
- C  $V_0 = V$
- D  $V_0 = \sqrt{2}V$

{ {<P=41><C=06><S=extension><T=MC><M=2><L=1><X=F><id=003> } }

4161003

**F E** The pointer deflection of an ammeter is proportional to the heating effect of the current. The ammeter is first calibrated by using a d.c. It is then used to measure an a.c. of r.m.s. value 10 A. What will be the reading of the ammeter?

- A 5 A
- B 7.07 A
- C 10 A
- D 14.1 A

{ {<P=41><C=06><S=extension><T=MC><M=2><L=1><X=F><id=004> } }

4161004


**E** Which of the following devices can operate normally with both a.c. and constant d.c.?

- (1) Heating filament
- (2) Transformer
- (3) Resistor
- A (1) and (2) only
- B (1) and (3) only
- C (2) and (3) only
- D (1), (2) and (3)

{{<P=41><C=06><S=extension><T=MC><M=2><L=1><X=H><id=005>}}

4161005

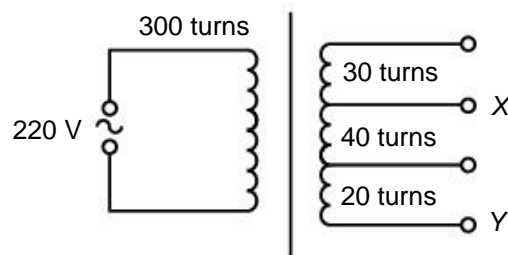**E** The following figure shows a multi-tapped transformer.




What is the voltage across XY?

- A 30 V
- B 44 V
- C 66 V
- D 90 V

{{<P=41><C=06><S=extension><T=MC><M=2><L=1><X=H><id=006>}}

4161006

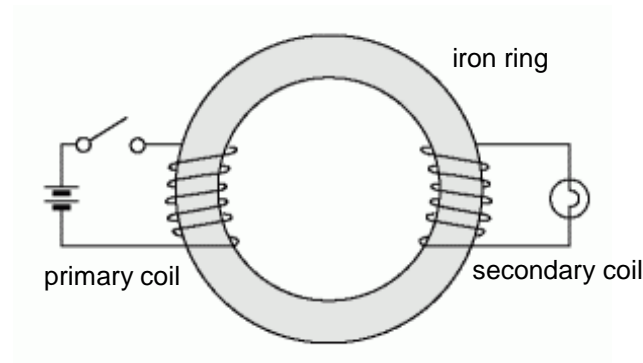**E** In the following figure, two coils are wound on an iron ring. The primary coil is connected to a battery and a switch; while the secondary coil is connected to a lamp.



When the switch is closed, what happens to the lamp in the secondary coil?

- A It lights up with gradually increasing brightness.
- B It flashes at a constant frequency.
- C It gives a flash of light.
- D It does not light up.

{{<P=41><C=06><S=extension><T=MC><M=2><L=1><X=H><id=007>}}

4161007

**E** Which of the following is **not** an effect of stepping up the voltage in a transmission cable?

- A The current in the cable is reduced.
- B The resistance of the cable is reduced.
- C The power loss in the cable is reduced.
- D Cable of lower cost can be used.

{{<P=41><C=06><S=extension><T=MC><M=2><L=1><X=H><id=008>}}

4161008


**E** Which of the following devices converts mechanical energy to electrical energy when it operates?

- A Battery
- B Generator
- C Motor
- D Transformer

{{<P=41><C=06><S=extension><T=MC><M=2><L=1><X=H><id=009>}}

4161009

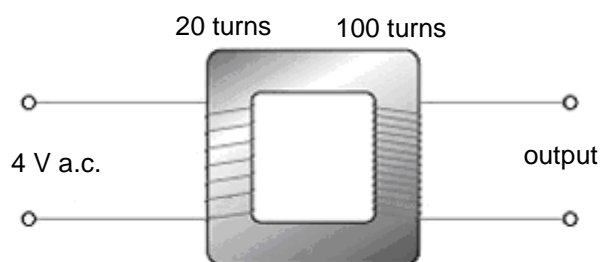**E** A 4-V a.c. supply is connected to the following transformer.




The current through the primary coil is 1 A and the power loss in the transformer is 0.8 W. What is the current through the secondary coil?

- A 0.04 A
- B 0.16 A
- C 0.2 A
- D 0.8 A

{{<P=41><C=06><S=extension><T=MC><M=2><L=1><X=H><id=010>}}


4161010

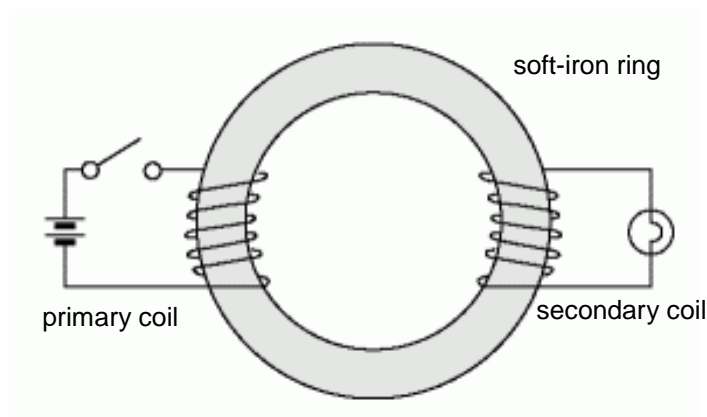**E** Two coils are wound on a soft-iron ring. The switch is turned on and then off.




Which of the following graphs correctly shows the variation of the induced current through the light bulb with time?


A

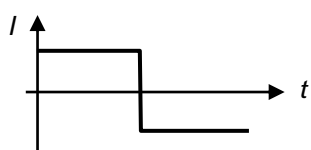


B

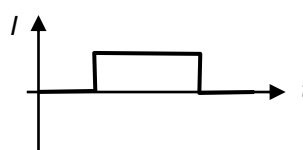

C

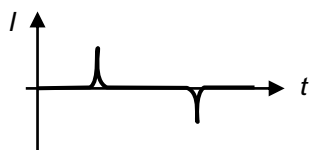

D

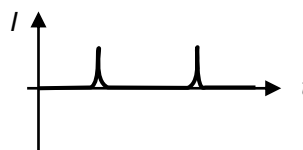

{{<P=41><C=06><S=extension><T=MC><M=2><L=1><X=H><id=011>}}

4161011

- E** Which of the following is an advantage of using high voltage for long distance power transmission?
- A The transmission speed can be increased.
  - B The needs of some heavy industries, which operate at high voltages, can be fulfilled.
  - C The power loss in the transmission cable can be reduced.
  - D Overhead power cables can be used.

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=F><id=012>}}

4161012

★

- F E** A heater of resistance  $R$  operates with a sinusoidal alternating current of peak value  $I$ . Which of the following expressions gives the mean power output of the heater?

- A  $\frac{1}{2} I^2 R$
- B  $\frac{1}{\sqrt{2}} I^2 R$
- C  $I^2 R$
- D  $\sqrt{2} I^2 R$

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=F><id=013>}}

4161013

★

**FE** A heater dissipates energy at a rate of 1 kW when it is connected to the mains. The peak value of the mains voltage is 340 V. The heater is then connected to a 340-V d.c. supply. What is the rate at which the heater dissipates energy now?

- A 0.5 kW
- B 1 kW
- C 1.41 kW
- D 2 kW

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=F><id=014>}}

4161014

★

**FE** A  $5\text{-}\Omega$  resistor dissipates energy at a rate of 20 W when it is connected to an a.c. supply. Which of the following is the peak value of the current?


- A 1.41 A
- B 2 A
- C 2.83 A
- D 4 A

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=015>}}

4161015

★

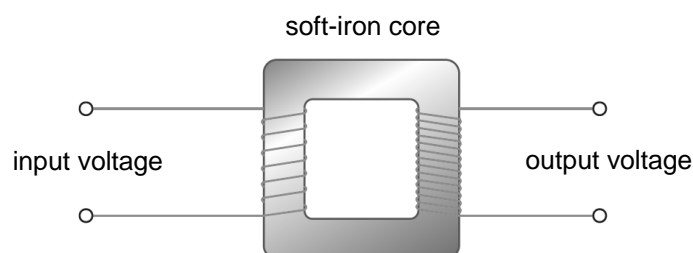**E** The following figure shows a simple transformer.



Which of the following method(s) can increase the efficiency of the transformer?

- (1) Use a laminated soft-iron core.
- (2) Replace the soft-iron core with highly conducting materials.
- (3) Cover the whole transformer with heat insulating material to reduce heat loss.

- A (1) only


- B (2) only
- C (1) and (3) only
- D (2) and (3) only

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=016>}}

4161016



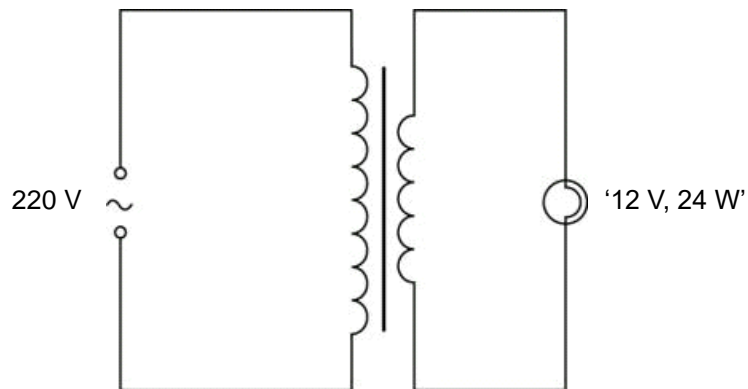- E** A light bulb rated at '12 V, 24 W' is connected to a transformer as shown in the following figure. An alternating voltage of 220 V is supplied to the primary coil and the primary current is 0.15 A.



If the light bulb operates at its rated value, what is the efficiency of the transformer?

- A 5.45%
- B 50%
- C 72.7%
- D Cannot be determined since the turns ratio of the transformer is not given.

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=017>}}

4161017



- E** The percentage loss of power in a transformer is 10%. The voltage across the primary coil and the current through the primary coil are 1.5 V and 5 A respectively. If the ratio of the number of turns in the primary and secondary coils is 1 : 20, what is the current through the secondary coil?

- A 0.225 A


- B 0.25 A  
C 0.5 A  
D 4.5 A

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=018>}}

4161018

★

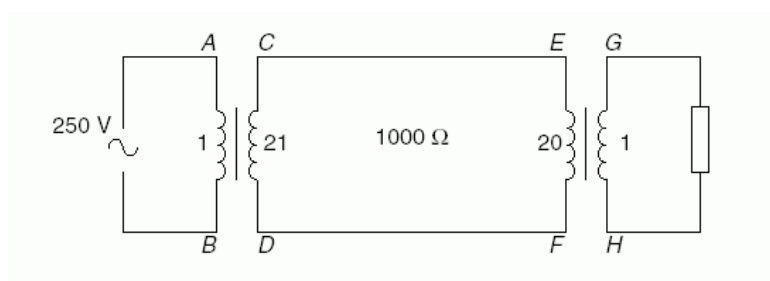- E** The following figure shows a power line for transmitting electrical power from a power station to a factory. The power line has a resistance of  $1\text{ k}\Omega$  and the current through the line is  $0.25\text{ A}$ .



If the transformers are 100% efficient, what is the voltage across  $GH$ ?

- A 200 V  
B 220 V  
C 250 V  
D 263 V

{{<P=41><C=06><S=extension><T=MC><M=2><L=3><X=F><id=019>}}

4161019

★★

- F E** The instantaneous value  $I$  (in A) of an alternating current at time  $t$  (in s) is given by the equation  $I = \sqrt{2} \sin 20\pi t$ . Which of the following descriptions are correct?

- (1) The frequency of the a.c. is 10 Hz.  
(2) The value of  $I$  varies between  $-\sqrt{2}\text{ A}$  and  $+\sqrt{2}\text{ A}$ .  
(3) The r.m.s. value of the current is 1 A.

- A (1) and (2) only  
B (1) and (3) only  
C (2) and (3) only  
D (1), (2) and (3)



{{<P=41><C=06><S=extension><T=MC><M=2><L=3><X=H><id=020>}}

4161020

★★

**E** A transformer works at an efficiency of 80%. The primary voltage is 100 V and the turns ratio is 20 : 1. If the resistance of the secondary circuit is  $50\ \Omega$ , what is the primary current?


- A 0.005 A
- B 0.006 25 A
- C 0.01 A
- D 2 A

{{<P=41><C=06><S=extension><T=MC><M=2><L=3><X=H><id=021>}}

4161021

★★

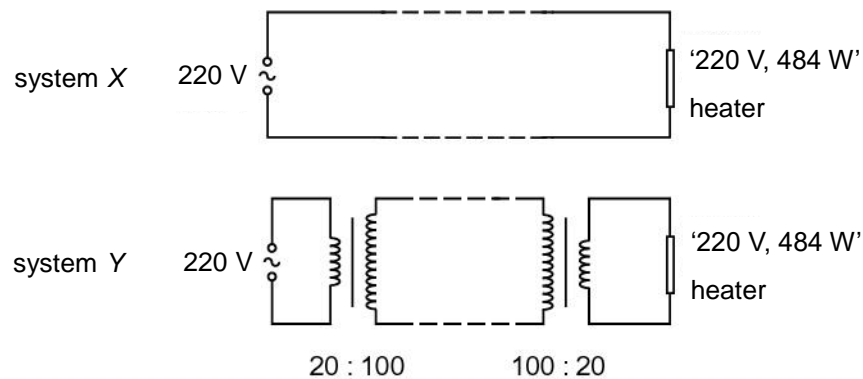**E** The figure below shows two different power transmission systems, X and Y.



The total resistance of the transmission cables in both systems are  $10\ \Omega$ . What is the ratio of the power loss in system X to that in system Y? Assume there is no power loss in transformers.

- A 10 : 1
- B 15 : 1
- C 20 : 1
- D 25 : 1

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=022>}}

4161022



E

**1st statement**

In a transformer, the primary current increases as the resistance of the secondary circuit decreases.

**2nd statement**

In a transformer, the secondary current increases as the resistance of the secondary circuit decreases.

{{<P=41><C=06><S= extension ><T=MC><M=2><L=2><X=H><id=023>}}

4161023



E

**1st statement**

A step-up transformer can step up both voltage and current.

**2nd statement**

The efficiency of a transformer can never be greater than 100%.

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=024>}}

4161024



E

**1st statement**

Power loss in transmission cables can be reduced if the electricity is transmitted at a high voltage.

**2nd statement**

Reducing the power loss in transmission cables can increase the efficiency of the transformers connected.

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=025>}}

4161025



E

**1st statement**

In a step-down transformer, the primary current is larger than the

**2nd statement**

A step-down transformer has fewer turns in the secondary coil than in the

secondary current.

primary coil.

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=026>}}

4161026

★

E

**1st statement**

A transformer is more efficient if  
thicker wires are used for its coils.

**2nd statement**

The energy loss in the coils of a  
transformer is reduced if thicker  
wires are used for its coils.

{{<P=41><C=06><S=extension><T=MC><M=2><L=2><X=H><id=027>}}

4161027

★

E

**1st statement**

A transformer is less efficient if  
the core is laminated.

**2nd statement**

The induced current in the core is  
reduced if the core is laminated.